

ECE 210 F00 Q7 11/09/00


NAME:

Honor Code:

KEY

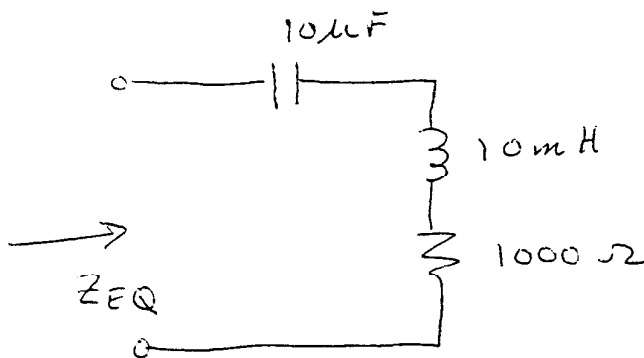1. Find The equivalent impedance of the network below. Use $f = 60$ Hz.

$$\omega = 2\pi f = 377 \frac{\text{rad}}{\text{Sec}}$$



$$Z_{EQ} = Z_C + Z_L + Z_R$$

$$= \frac{-j}{\omega C} + j\omega L + R$$

$$= \frac{-j}{(377) \cdot (10 \times 10^{-6})} + j(377)(.01) + 1000$$

$$= \underline{(1000 - 261.48j) \Omega}$$